

EECS 3420 Electronics II
Special Problem Set Solutions

Name _____

For each of the following BJT's (Q1-Q8), voltages with respect to circuit common are given. Determine which of the four modes of operation it is in.

