

Jaeger 3rd ed


13.99

$$K_n = 500 \mu\text{A}/\text{V}^2$$

$$\lambda = \frac{1}{50\text{V}}$$

$$I_D = 100 \mu\text{A}$$

$$V_{DS} = 5\text{V}$$

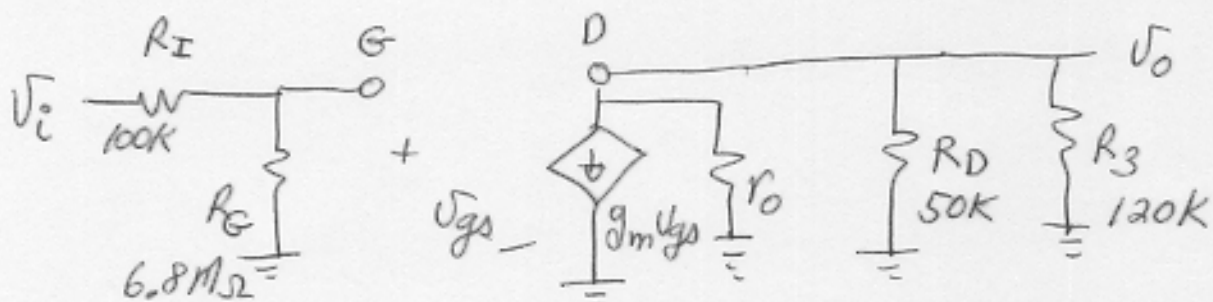

$$g_m = \sqrt{2 K_n I_D (1 + \lambda V_{DS})} = 332 \mu\text{S} \quad \left(\approx \sqrt{2 K_n I_D} \right) = 316 \mu\text{S}$$

$$r_o = \frac{1 + \lambda V_{DS}}{2 I_D} = 550 \text{K}\Omega \quad \left(\approx \frac{1}{\lambda I_D} = 500 \text{K}\Omega \right)$$

$$A_v \equiv \frac{v_o}{v_i} = \left(\frac{R_G}{R_I + R_G} \right) (-g_m) (r_o \parallel R_D \parallel R_L)$$

$$= (0.986) (-332 \mu\text{S}) (33.2 \text{K}\Omega)$$

$$= -10.8 \quad (+21\text{dB})$$