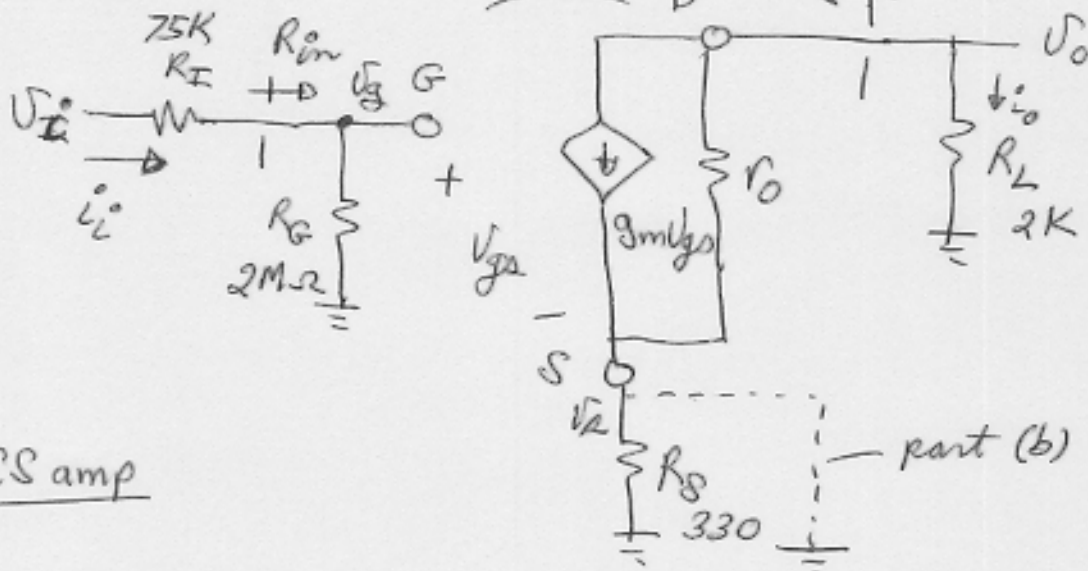


Jaeger 3rd ed

14.8



$$\frac{m_1}{g_m = 5 \text{ mS}}$$

$$r_o = 10 \text{ K}$$

$$\mu = g_m r_o = 50$$

CS amp

$$v_o = v_{gs} \frac{(-g_m r_o) R_L}{R_S + R_L + r_o}$$


$$\left( \approx -v_{gs} g_m (r_o \parallel R_L) \right)$$

$$v_s = v_{gs} \frac{(+g_m r_o) R_S}{R_S + R_L + r_o}$$

$$v_{gs} = v_g - v_s \quad \underline{\text{so}}$$

$$v_{gs} = v_g - v_{gs} \frac{(g_m r_o) R_S}{R_S + R_L + r_o}$$
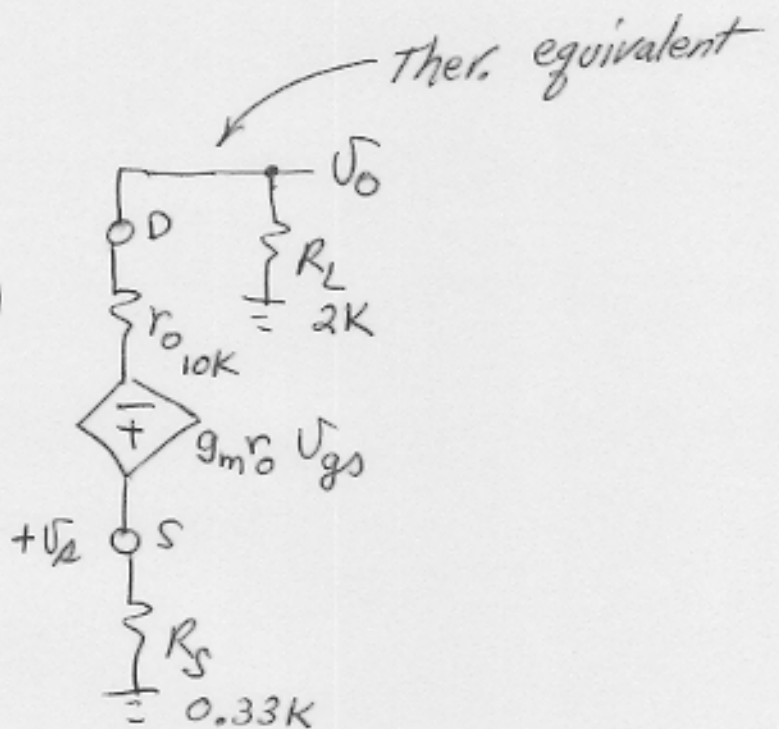
$$\Rightarrow v_{gs} = v_g \frac{R_S + R_L + r_o}{R_S + R_L + r_o + g_m r_o R_S} \approx v_g \frac{1}{1 + g_m R_S}$$



Jaeger 3rd ed.

14.8 cont

$$\therefore \frac{V_o}{V_g} = \frac{-g_m r_o R_L}{R_S + R_L + r_o + g_m r_o R_S} \approx \frac{-g_m (R_L \parallel r_o)}{1 + g_m R_S}$$

$$\therefore A_V \equiv \frac{V_o}{V_i} = \frac{V_g}{V_i} \frac{V_o}{V_g} = \frac{R_G}{R_I + R_G} \frac{-g_m r_o R_L}{R_S + R_L + r_o + g_m r_o R_S}$$

$\therefore A_V = -3.34$  (exact), OR  $-3.03$  (approx)


(a)  $R_{in} = R_G = 2 M\Omega$

$$A_i = \frac{i_o}{i_i} = \frac{V_o}{V_i} \frac{R_I + R_G}{R_L} = -3465$$

$$R_{out} = \frac{V_t}{i_t} = R_S + (1 + g_m R_S) r_o$$

$$\approx (1 + g_m R_S) r_o$$

$$R_{out} = 26.8 K\Omega$$

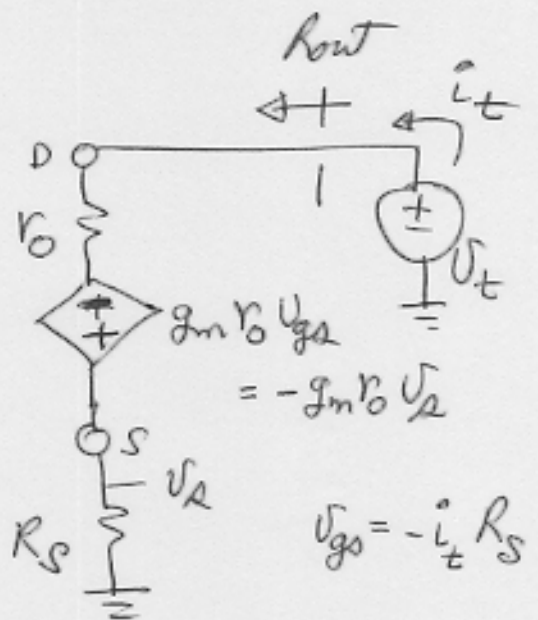

(b) let  $R_S \rightarrow 0$

$$A_V = -8.03$$

$$R_{in} = 2 M\Omega$$

$$A_i = -8333$$

$$R_{out} = r_o = 10 K\Omega$$

— finding  $R_{out}$  —