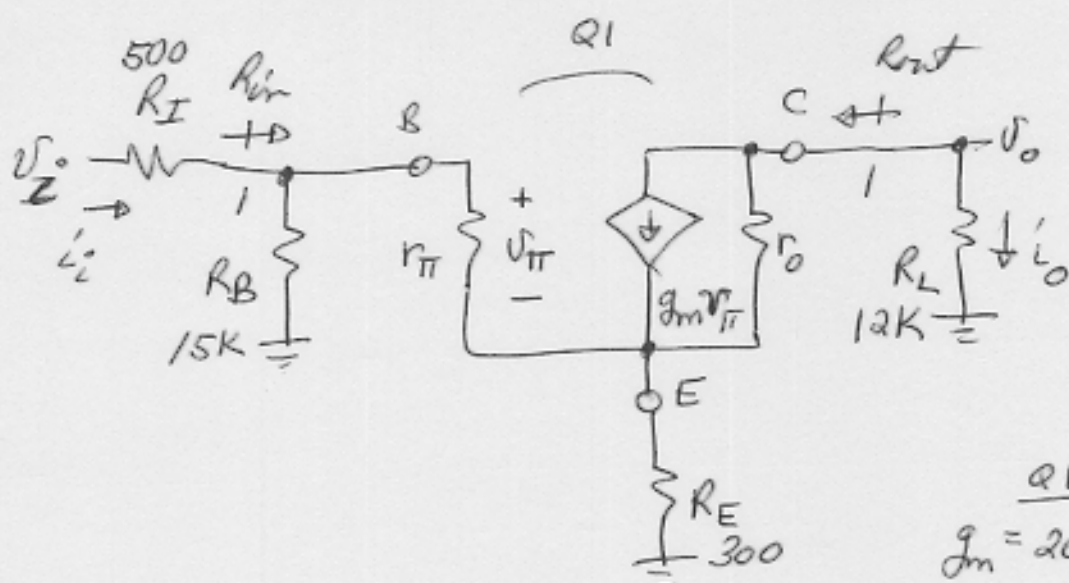


14.9



CE amp

Reasonable Approximations

$$v_o \approx -g_m (r_o \parallel R_L) v_{\pi}$$

Q1

$$g_m = 20 \text{ mS}$$

$$\beta_o = 75$$

$$r_o = 100 \text{ K}$$


$$r_{\pi} = \frac{\beta_o}{g_m} = 3750 \text{ } \Omega$$

$$[(\beta_o) - R_E = 620]$$

$$v_{\pi} = v_b \frac{r_{\pi}}{r_{\pi} + (1 + \beta_o) R_E}$$

$$= v_b \frac{r_e}{r_e + R_E} = v_b \frac{1}{1 + \frac{1 + \beta_o}{\beta_o} g_m R_E}$$
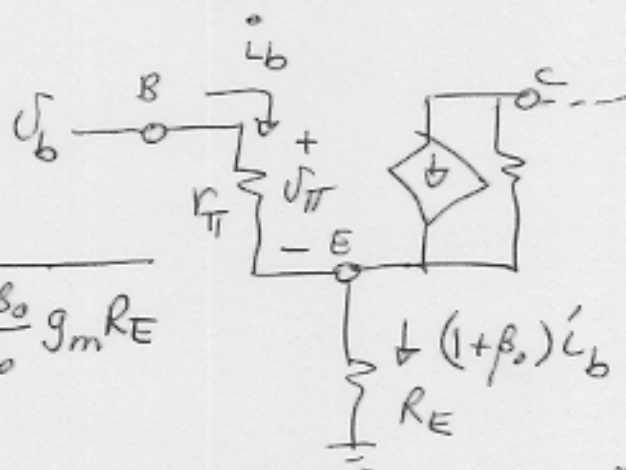
$$v_{\pi} \approx \frac{v_b}{1 + g_m R_E}$$



$$r_e \equiv \frac{r_{\pi}}{1 + \beta_o}$$


$$R_{in} = R_B \parallel [r_{\pi} + (1 + \beta_o) R_E]$$

$$v_b = v_i \frac{R_{in}}{R_{in} + R_I}$$

Jaeger 3rd ed

14,9 cont

Finding Rout

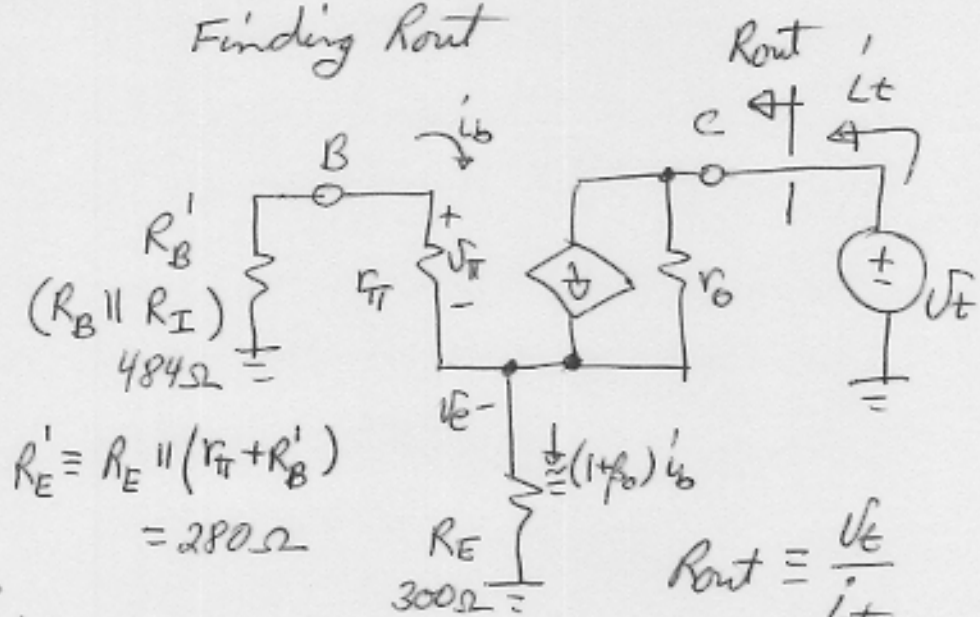

$$v_{\pi} = - \frac{r_{\pi}}{R_B' + r_{\pi}} R_E' i_t$$

$$v_e = R_E' i_t$$

$$v_o = R_E' i_t + (i_t - g_m v_{\pi}) r_o = \left[R_E' + r_o + \frac{g_m r_o r_{\pi} R_E'}{R_B' + r_{\pi}} \right] i_t$$

$$\circ \circ R_{out} \equiv \frac{v_o}{i_t} = R_E' + r_o + g_m R_E' \frac{r_{\pi}}{R_B' + r_{\pi}} r_o = 596 K\Omega$$

$$\approx \left(1 + g_m R_E' \frac{r_{\pi}}{R_B' + r_{\pi}} \right) r_o \approx (1 + g_m R_E') r_o = 660 K\Omega$$

$$(a) A_v \equiv \frac{v_o}{v_i} \approx \frac{R_{in}}{R_I + R_{in}} \frac{-g_m (r_o \parallel R_L)}{1 + g_m R_E} = -29 \quad (+29 dB)$$

$$R_{in} = R_B \parallel (r_{\pi} + (1 + \beta_o) R_E) = 9.6 K\Omega$$

$$A_i \equiv \frac{i_o}{i_i} = A_v \frac{R_I + R_{in}}{R_L} = -24 \quad (+28 dB)$$

$$R_{out} \approx (1 + g_m R_E') r_o = 660 K\Omega$$

