
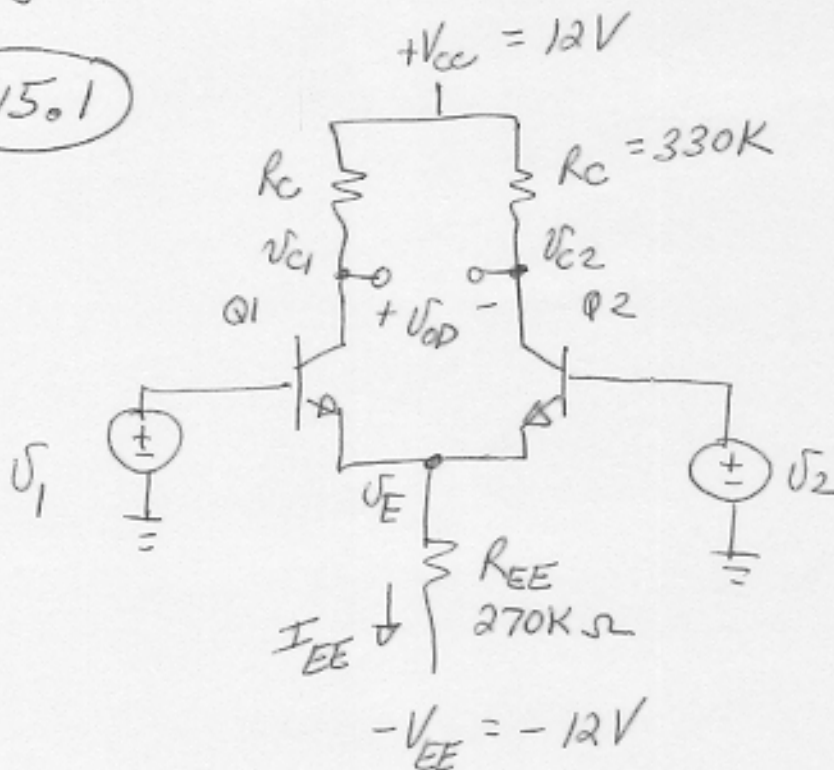


15.1

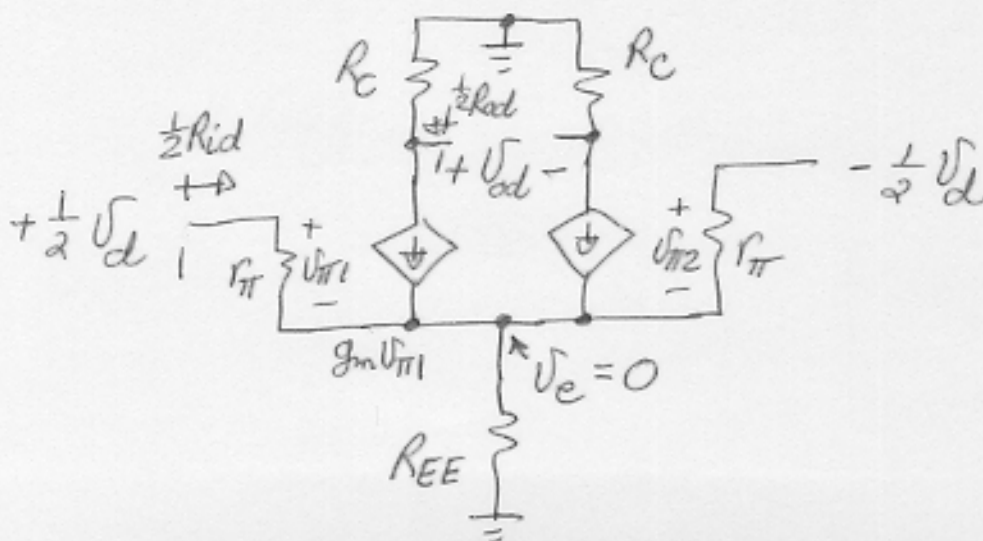

Q-points for  $V_1 = V_2 = 0$ .  $V_E \approx -0.7V$ .  $I_{EE} \approx \frac{11.3V}{R_{EE}} = 42\mu A$   
 so, for each transistor

(a)  $I_E = 21\mu A$ ,  $I_B = 207nA$ ,  $I_C = 21\mu A$ ,  $V_{CE} = 12 + 0.7 - I_C R_C = +5.9V$   
 and  $V_{OD} = 0$ .



for  
 $I_C = 21\mu A$   
 $\beta_0 \approx 100$

$g_m = 840\mu S$   
 $r_{\pi} = 119K\Omega$

Jaeger 3rd ed

15.1 cont

gain (diff)  $\frac{1}{2} v_{od} = -g_m R_C \left( \frac{1}{2} v_d \right)$


so  $A_d = \frac{v_{od}}{v_d} = \pm g_m R_C = \pm 277$

(b)

(gain sign easily reversed by interchanging the two input or output terminals)

$\frac{1}{2} R_{id} = r_{\pi} \Rightarrow R_{id} = 2r_{\pi} = 238 \text{ K}\Omega$

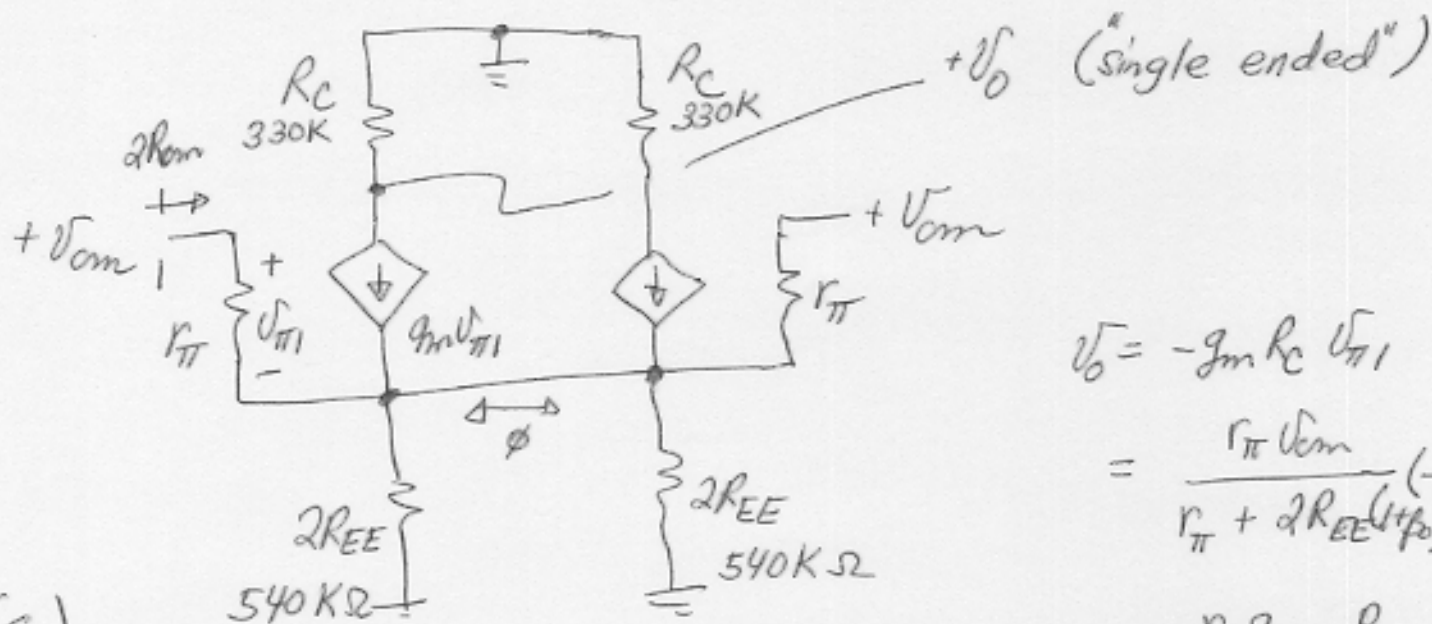$\frac{1}{2} R_{od} = R_C \Rightarrow R_{od} = 2R_C = 660 \text{ K}\Omega$



$$v_o = -g_m R_C v_{\pi 1}$$

$$= \frac{r_{\pi} v_{cm}}{r_{\pi} + 2R_{EE}(1+\beta_0)} (-g_m R_C)$$

$$\approx \frac{-r_{\pi} g_m R_C v_{cm}}{2 R_{EE} (1+\beta_0)}$$

(c)

$A_{cm} = \frac{v_o}{v_{cm}} \approx \frac{-R_C}{2R_{EE}} = -0.61$

$A_d = \frac{v_o}{v_d} = \pm \frac{1}{2} g_m R_C = \pm 138 = \frac{-\alpha R_C}{2 R_{EE}} v_{cm}$

$CMRR = \left| \frac{A_d}{A_{cm}} \right| = 227 (+47\text{dB})$

$R'_{icm} \approx R_{EE}(1+\beta_0) = 27 \text{ M}\Omega$