

Jaeger 3rd ed

16.22


$$I_C = 0.25 \text{ mA}$$

$$V_{CE} = 12 \text{ V}$$

$$\beta_0 = 100$$


$$R_1 = 100 \text{ K}$$

$$R_2 = 300 \text{ K}$$

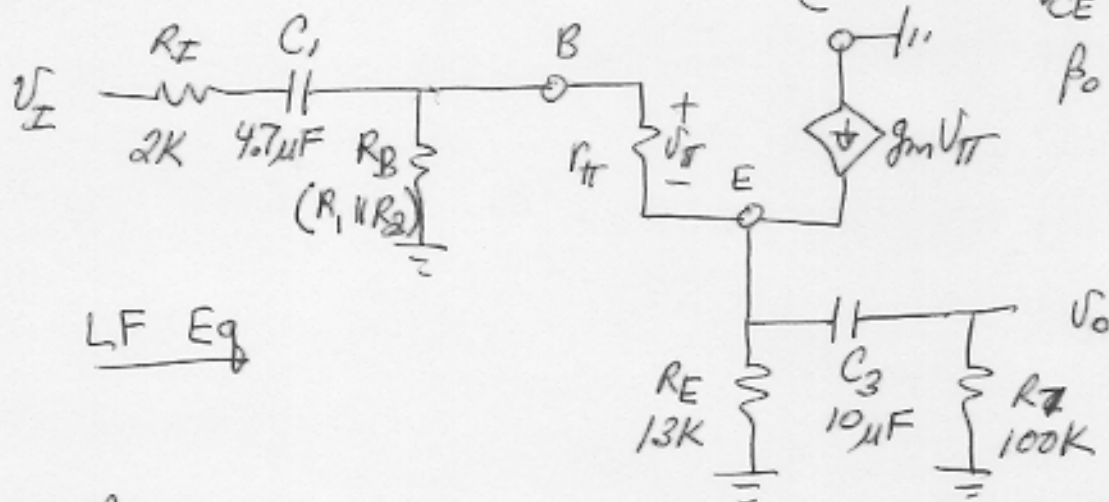

LF Eq

(a)

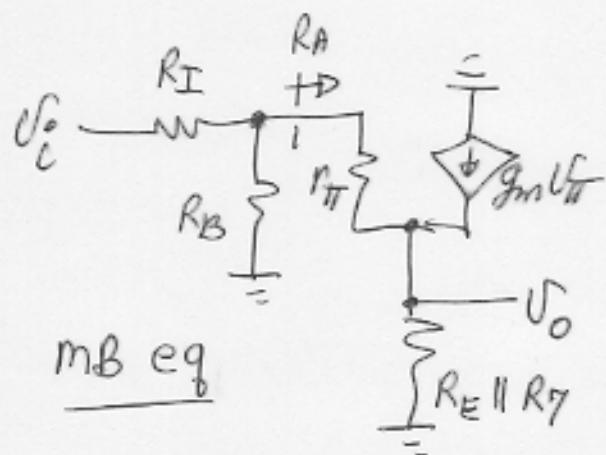

mb eq

$$g_m = \frac{I_C}{V_T} = 10 \text{ mS}$$

$$r_{\pi} = \frac{\beta_0}{g_m} = 10 \text{ K}\Omega$$


$$r_e = 99.0 \Omega$$

$$(b) A_m = \left. \frac{v_o}{v_i} \right|_{\text{midband}} = \frac{R_B \parallel [r_{\pi} + (1 + \beta_0)(R_E \parallel R_7)] (R_E \parallel R_7)}{R_I + R_B \parallel [r_{\pi} + (1 + \beta_0)(R_E \parallel R_7)] (R_E \parallel R_7) + r_e}$$

$$= +0.96$$

16.22 cont


Use Method S, C, time constants

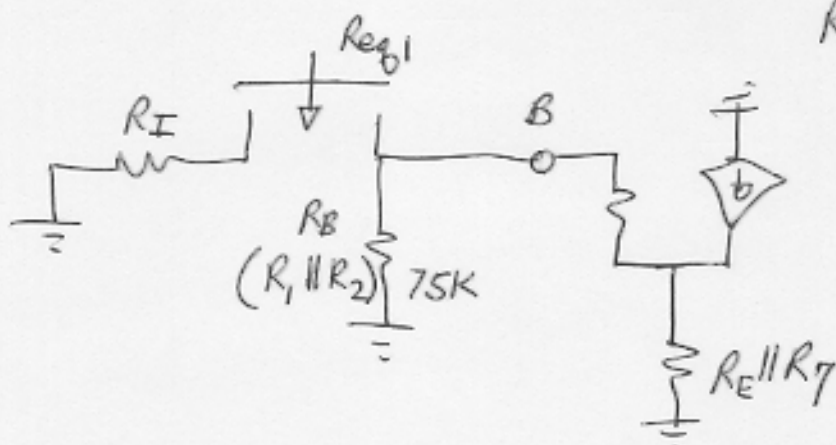

$$R_{eq1} = R_I + R_B \parallel \left[ r_{\pi} + (1 + \beta_0) R_E \parallel R_7 \right]$$

$$= 72.49 \text{ K}\Omega$$
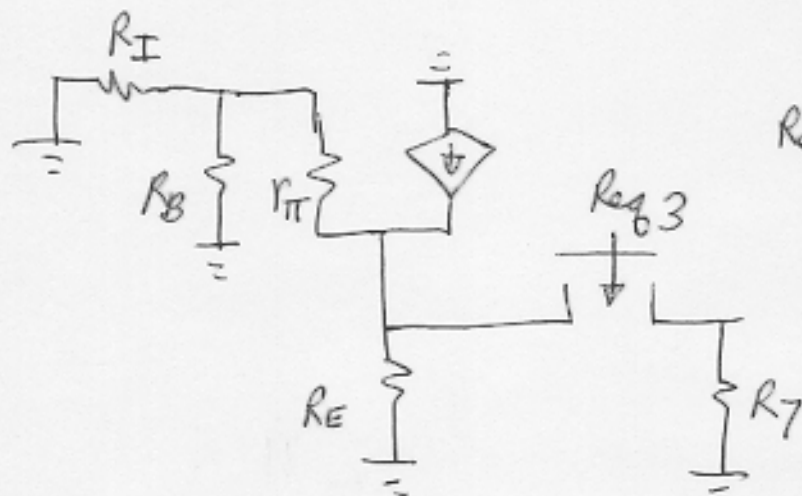
$$\left( \frac{1}{R_{eq1} C_1} \right) = 2.94 / \text{sec}$$



$$R_{eq3} = R_7 + R_E \parallel \left[ \frac{(R_I \parallel R_B) + r_{\pi}}{1 + \beta_0} \right]$$

$$= 100.1 \text{ K}\Omega$$

$$\left( \frac{1}{R_{eq3} C_3} \right) = 1.00 / \text{sec}$$

$$\omega_L \approx 3.94 \text{ rad/s}$$

$$f_L = 0.63 \text{ Hz}$$