


prob 16.53 in Jaeger 3rd edition (compare prob 16.52)

PSpice simulation using a steady-state AC frequency sweep produces a midband gain of +39 dB,  $f_L = 0$ , and  $f_H = 5.52$  MHz. The corresponding hand-worked values, using Miller's theorem in an approximate way, are +39 dB, 0, and 6.04 MHz.

PSpice simulation of the complex input impedance produces the following numbers, also compared with the approximate results from prob. 16.52:


Frequency	prob 16.52 Input Z mag (approx)	prob 16.52 Input Z phase (approx)	prob 16.53 Input Z mag (PSpice)	prob 16.53 Input Z phase (PSpice)
0 Hz	2750 $\Omega$	0 deg		
1 kHz	2750 $\Omega$	0 deg		
50 kHz	2,739 $\Omega$	-5 deg	2738 $\Omega$	-5 deg
1 MHz	1341 $\Omega$	-52 deg	1337 $\Omega$	-51 deg
10 MHz	292 $\Omega$	-28 deg	307 $\Omega$	-26 deg
100 MHz	251 $\Omega$	-3 deg	269 $\Omega$	-4 deg

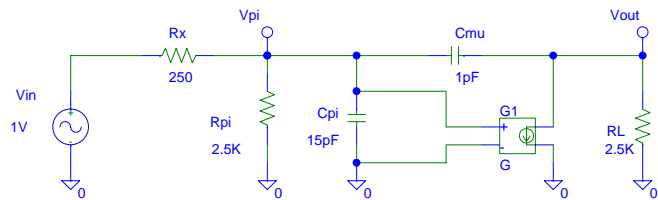
There is excellent agreement up to, and beyond, the frequency of the dominant pole at 5.5 MHz. The approximate use of Miller's theorem explains the discrepancy at 100 MHz.



Jaeger 3rd edition, Prob 16.53 (see prob 16.52)

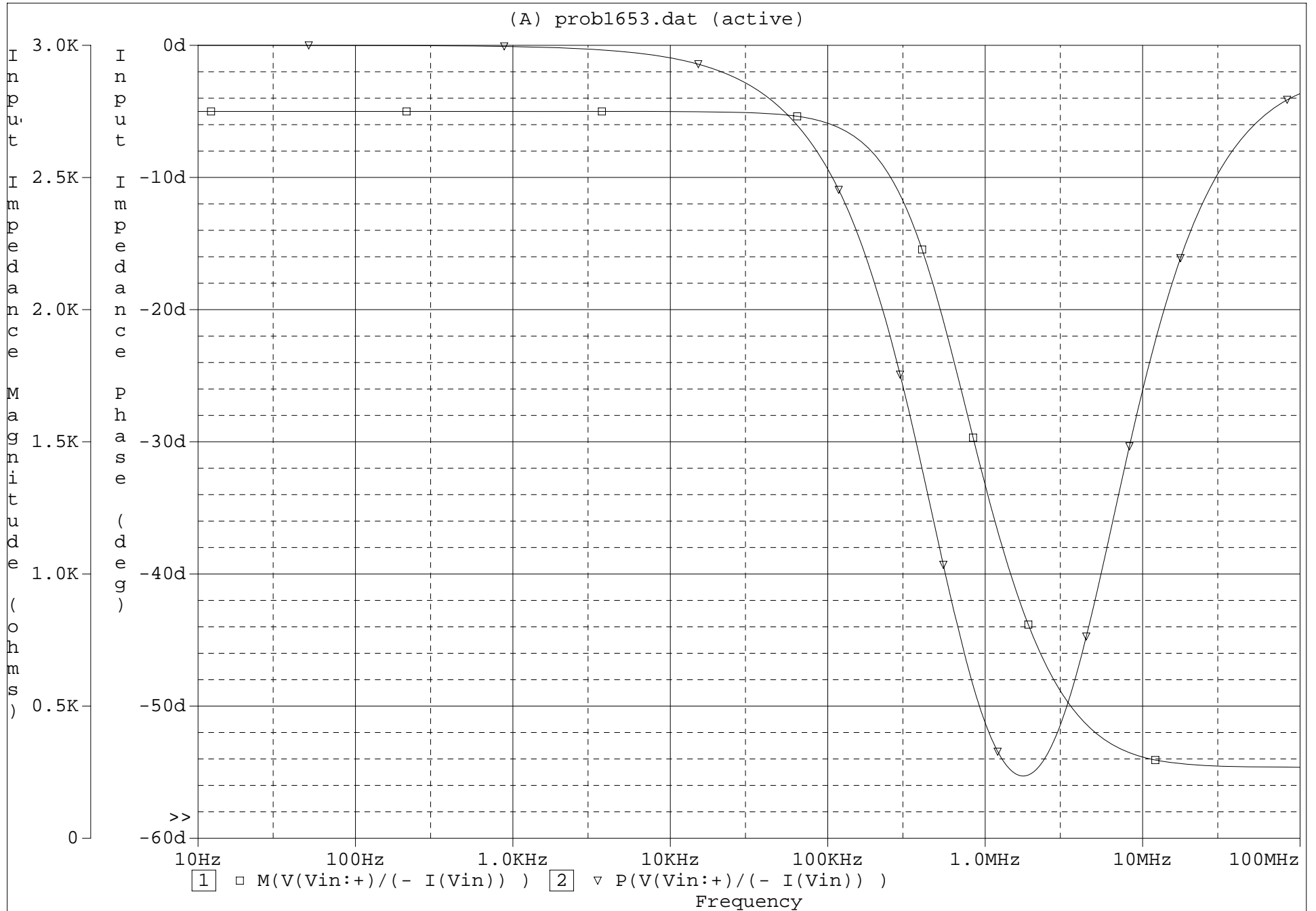Vin is an AC source, 1V. Analysis is AC sweep; 0-100MHz. Results are AC steady-state input impedance, and voltage transfer function.



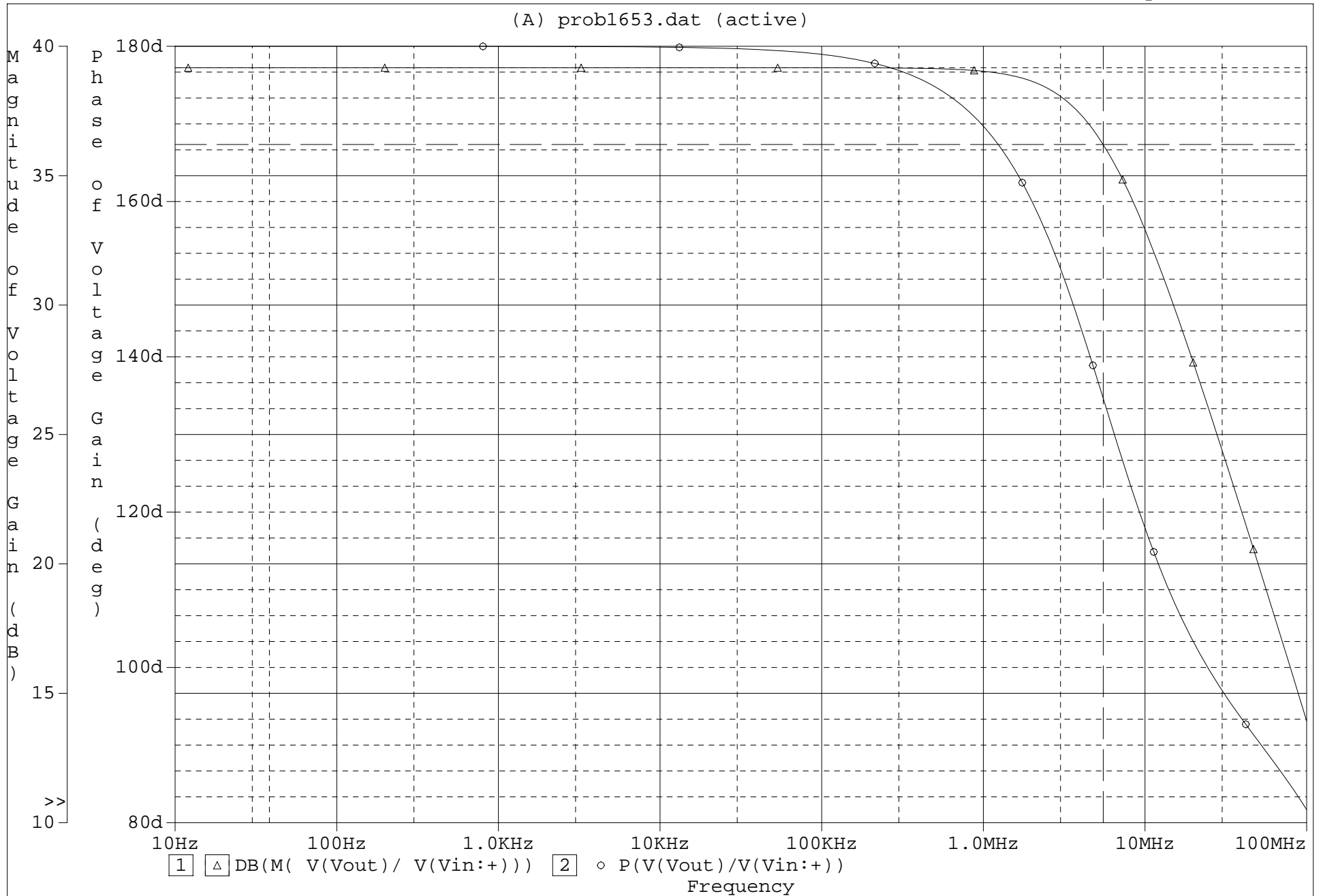

A1:(38.312,39.172) A2:(5.5165M,36.204) DIFF(A):(-5.5165M,2.9679)